



Electricity and Magnetism

Name: _____

Date: _____

Grade: Grade 3

Part A: Fill in the Blank

Write the missing word or number on each line.

1. A _____ circuit has no gaps so electricity flows all the way around.
2. An _____ circuit has a break, so the bulb will not light.
3. A material that lets electricity flow through it is called a _____.
4. A material that stops electricity from flowing is called an _____.
5. A _____ can open or close a circuit by pressing or flipping it.
6. Copper is a metal that is a very good _____ of electricity.
7. Wires are usually covered with plastic to act as an _____.
8. The part of a circuit that gives off light is the _____.
9. A _____ is the power source that pushes electricity around a circuit.

Part B: Matching

Match each item on the left to the correct answer on the right.

1. Match each item to its correct answer.

Closed circuit	→ _____	A complete loop where electricity flows
Open circuit	→ _____	A broken path so the bulb stays off
Conductor	→ _____	Copper wire that carries electricity
Insulator	→ _____	Rubber that stops electricity from passing

Part A: Fill in the Blank

Write the missing word or number on each line.

1. A closed circuit has no gaps so electricity flows all the way around.
2. An open circuit has a break, so the bulb will not light.
3. A material that lets electricity flow through it is called a conductor.
4. A material that stops electricity from flowing is called an insulator.
5. A switch can open or close a circuit by pressing or flipping it.
6. Copper is a metal that is a very good conductor of electricity.
7. Wires are usually covered with plastic to act as an insulator.
8. The part of a circuit that gives off light is the bulb.
9. A battery is the power source that pushes electricity around a circuit.

Part B: Matching

Match each item on the left to the correct answer on the right.

1. Match each item to its correct answer.

Closed circuit	→	<u>A complete loop where electricity flows</u>	A complete loop where electricity flows
Open circuit	→	<u>A broken path so the bulb stays off</u>	A broken path so the bulb stays off
Conductor	→	<u>Copper wire that carries electricity</u>	Copper wire that carries electricity
Insulator	→	<u>Rubber that stops electricity from passing</u>	Rubber that stops electricity from passing